 


# Development of solid state amplifiers at ESRF




Cavity combiner prototype

Michel Langlois

*\* This work, carried out within the framework of the CRISP project, has received research funding from the EU Seventh Framework Programme, FP7.*
 
# RF combining : the cavity combiner


We developed a cavity combiner which could couple up to 132 RF modules. Input coupling is provided by loops on the periphery. Output coupling is capacitive and excite the fundamental rectangular waveguide mode.



E field

E010 mode


Note: a coaxial output is possible

 

H field


# Cavity combiner: the prototype

The waveguide short-circuit can be moved

 


Coupling to the capacitive post can be trimmed

input coupling seen from inside

 


The width and the height of the loops can be adjusted.

# cavity combiner: low level results

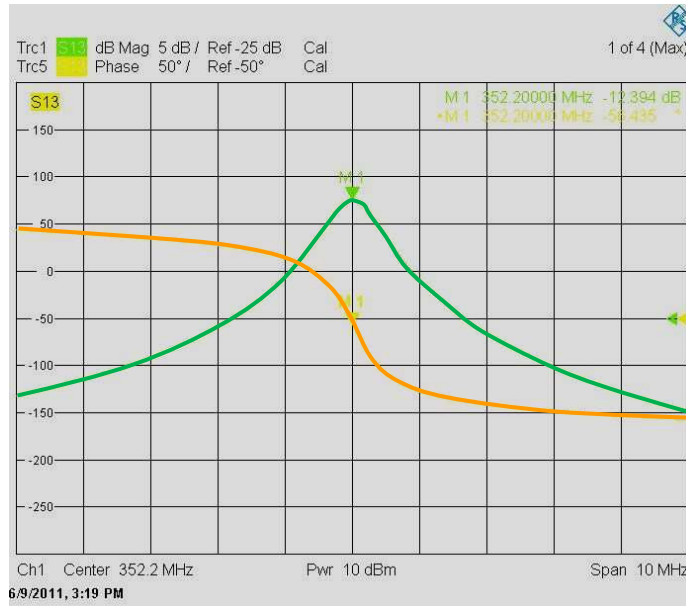

S31 plot measured with a NWA  
1 being the waveguide output port

 S11 plot measured with a NWA.  
The output can be matched with 7 to 18 inputs without changing the loop size.




# Cavity combiner: issues

- The behaviour with power has not yet been tested.
- There is a discrepancy on  $S_{1i}$ , depending on the  $i$  loop position. The loop size must vary with position.

We adjusted washers on the loops to vary their heights and got close values for all  $S_{1i}$

### $S_{1i}$ measurements

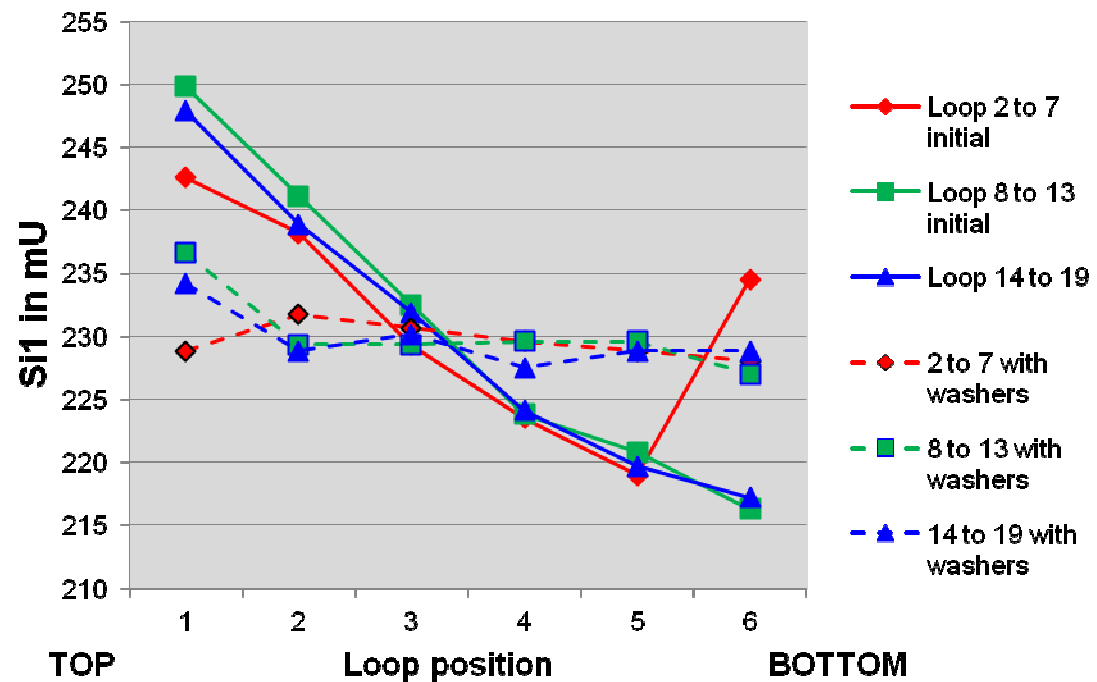

## The cavity combiner : losses

### Theory:

Most of the losses are due to the current in the cylindrical wall.


We computed 1.35 kW for 75 kW output (conductivity:  $5 \cdot 10^7$  S/m). It does not depend heavily on the number of input loops. It means 0.08 dB insertion loss.

### Low level measurements:


$$\left| \sum_{i=2}^{19} S_{i,1} \right| = \sqrt{17.23}$$

The theoretical value would be  $\sqrt{18}$

 A dubious contact was seen on the movable short circuit, but straightening the waveguide sagging did not change  $\sum S_{1,i}$ .


 
# cavity combiner: modules implementation



The cavity is made of 22 columns bearing 6 RF modules each. On this picture, the AC/DC converters are located on the same cooling plate. This option is no longer considered.

RF modules, individually shielded


AC/DC converter

The wings constitute the cylindrical cavity wall

## Cavity combiner: modules implementation

For the 10kW first step, the cavity is fitted with 3 adjacent (or not) “wings”. Each of them is equipped with 6 transistor amplifiers. They are all water cooled. The water feeding circuit has not been designed yet. It cannot use the ESRF deionized water circuit, because aluminum is forbidden on this loop.

RF modules globally shielded

 




## Cavity combiner: test fixture

For test purpose only, a 7/16 output connector can be fitted on the circulator output. A N connector is fitted at the input.

N input connector


7/16 output connector

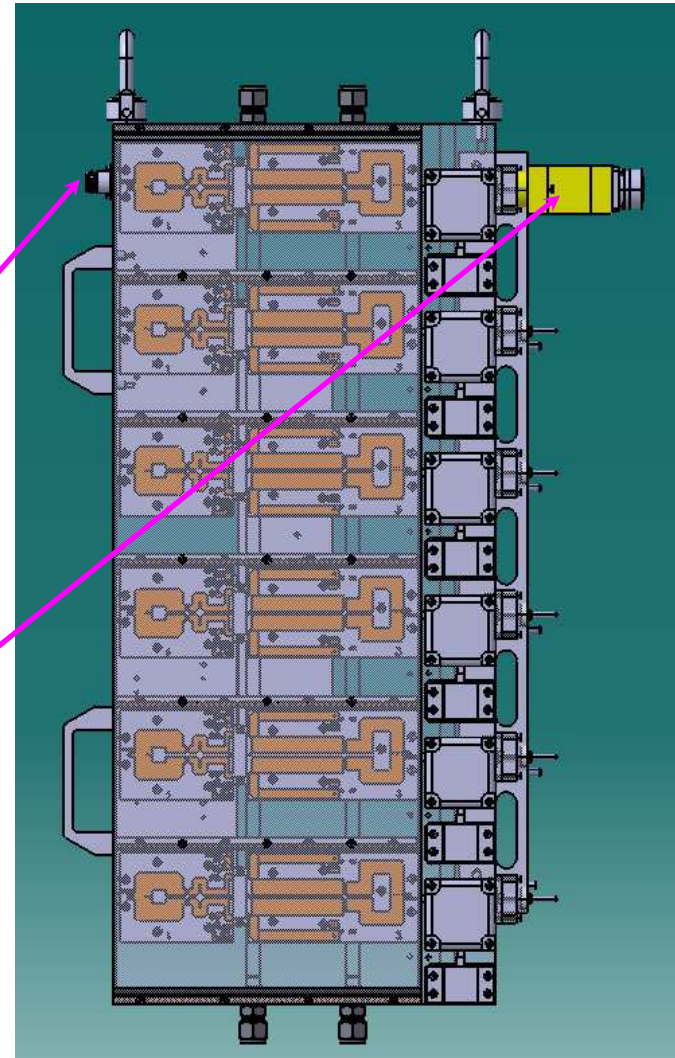

## Cavity combiner: RF distribution

RF distribution is made with printed Wilkinson dividers to avoid connectors and cables. The 2 ways splitter is a delta Wilkinson, and the 3 ways is star connected.



RF distribution

 

# Cavity combiner: 2 ways Wilkinson divider




It uses 1.6mm thick RT5870 (low  $\epsilon$ ) to avoid too thin lines and losses. The narrow shape helps minimizing the area, and hence the cost.

100  $\Omega$  resistor

  
 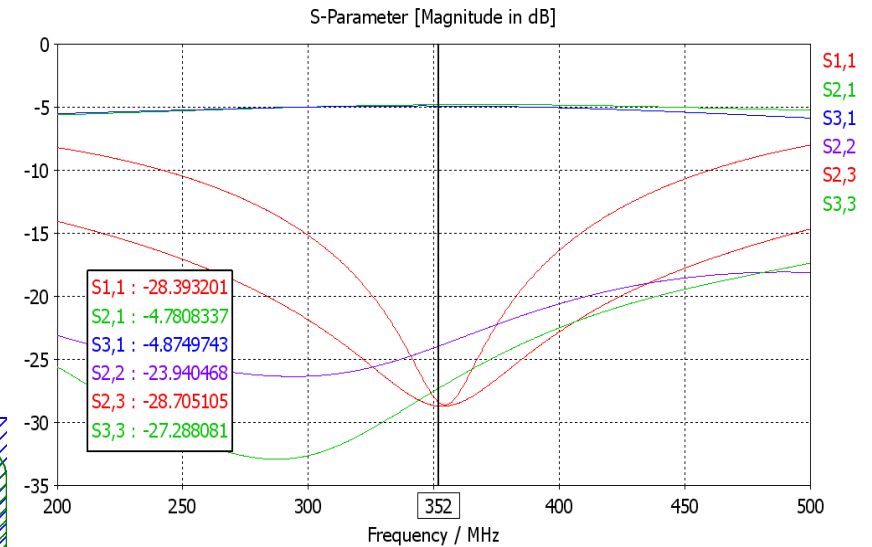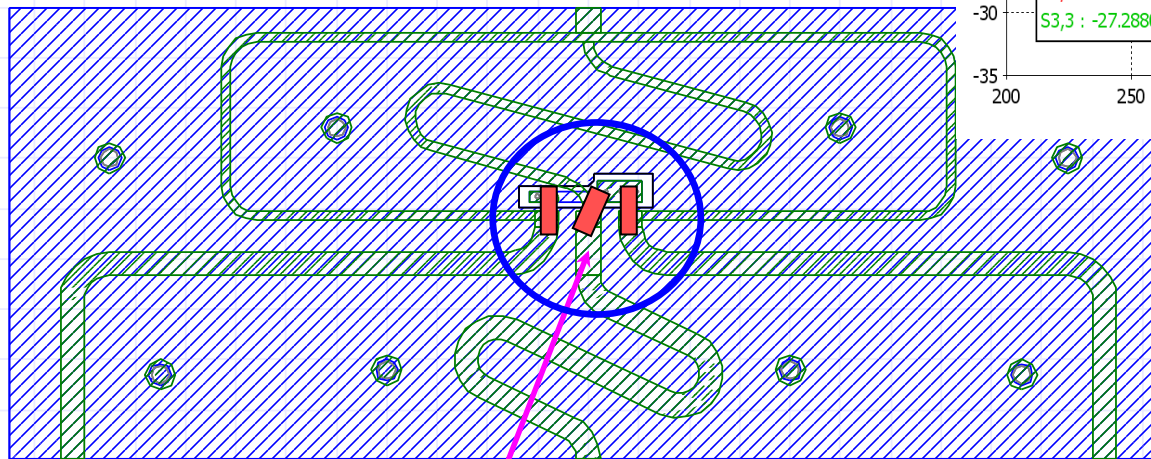
# Cavity combiner: 3 ways Wilkinson star divider

Same RT5880 (low  $\epsilon$ ) substrate. The strange shape helps minimizing the area, and hence the cost.




50  $\Omega$

resistors

Top  
Bottom

# The RF module: Scheme

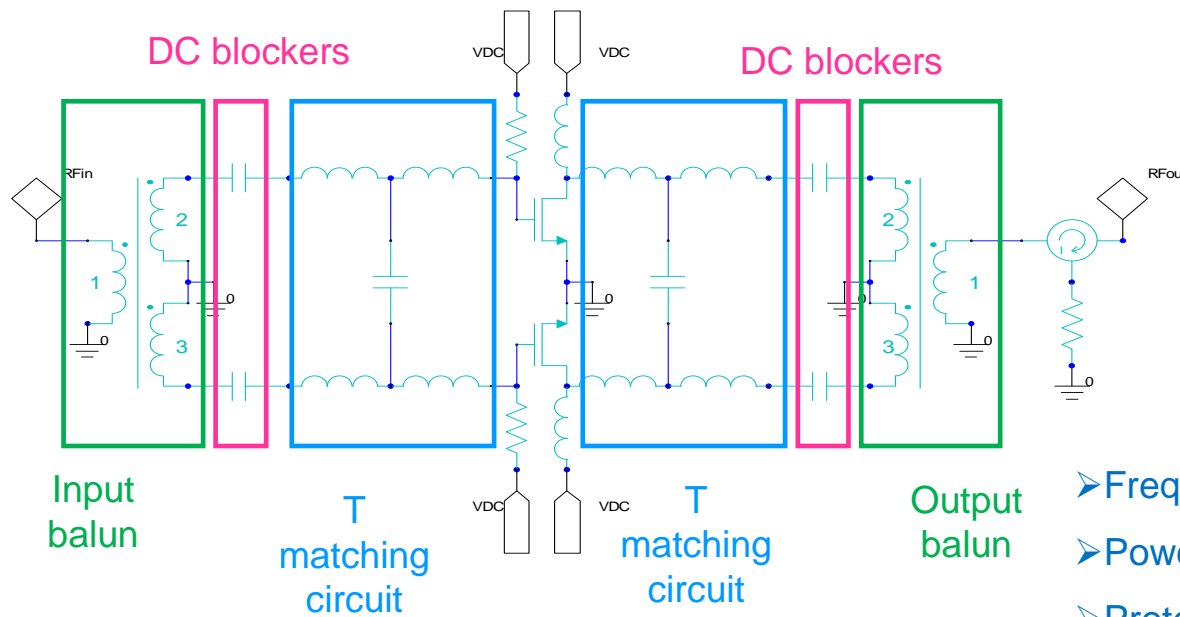

## Targets :

- Frequency: 352.2 MHz
- Power: 800 W C.W. at -1dB compression
- Protected against V.S.W.R
- Bandwidth: >2MHz at 0.2 dB
- Drain efficiency: 70% at full power
- Low quiescent current
- **Cost effective**

# The RF module: design options

## Avoidance of components needing manual intervention

- No variable capacitors
- Suspended printed planar baluns
- No trimmer except for gate bias
- No RF chokes


## Transistor choice: LDMOS 50V

- NXP BLF578
- FREESCALE MRF6VP41KH
- Ruggedized version of the formers

# Planar printed baluns


invented by Mr J.Bouny for MOTOROLA

unbalanced

 


balanced

Balanced on top  
Unbalanced on bottom

 


NXP design

 The cooling plate has to be milled and the balun is difficult to cool




## The RF module: input

V1

 

The input circuit printed circuit was OK from the start. The 2<sup>nd</sup> version has two bias voltage sources made from the drain voltage.



V3

 



# The RF module: output

Confidential

  


V1

Substrate  $\lambda=0.24\text{W/m}\cdot\text{K}$


Overheating of the output balun and its matching capacitors.
 
# The RF module output circuit: 578OutV21



V21

 High conductivity substrate  
No capacitor on the balun



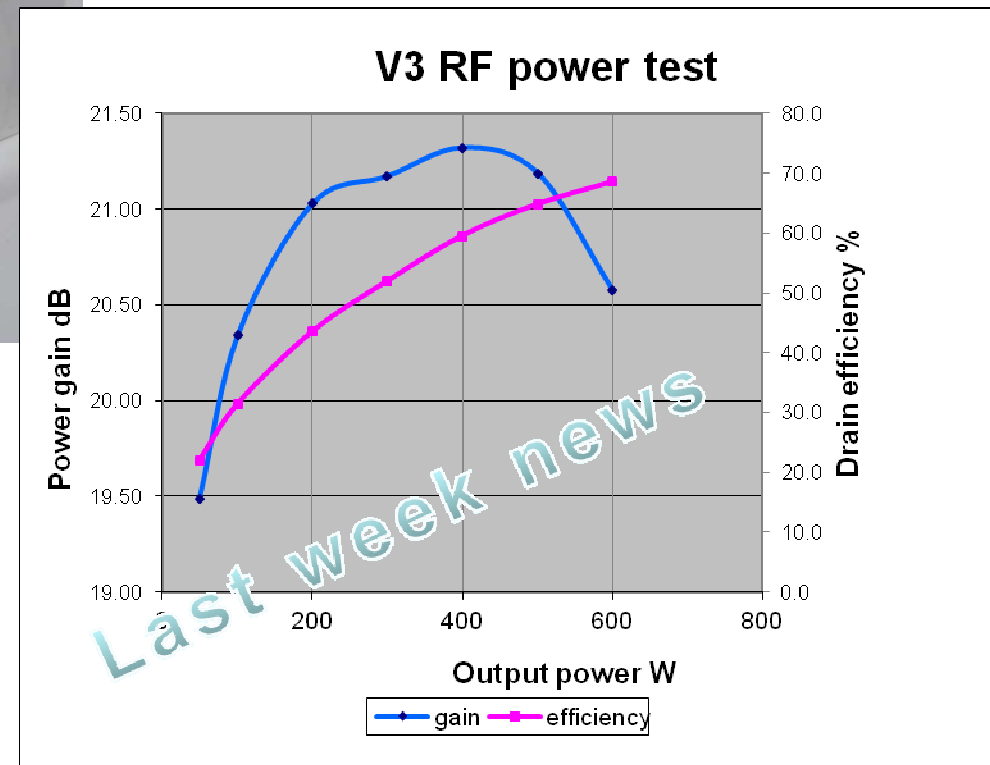
## The RF module output circuit: 578V3V3



V3

RF drain chokes have been replaced with “quarter wave” transmission lines. Very few components are left, all of them CMS and prone to automated manufacturing in Europe.



## The RF module: issues

- The results shown were obtained with the NXP transistor. It has to be repeated with the FREESCALE MOSFET.
- The power limitation comes from the transistor ESD protection diode, which conducts as soon as the input power reaches 6.4 W. This is probably the reason for the early saturation of the V3 version. The XR ruggedized version should not exhibit this drawback.
- The reproducibility has not been checked yet.
- The output matching capacitor is hot. Long runs have to be performed to make sure these temperatures are acceptable.

## 578V3V3 : prices

Bill of material:

€€€€!!!

For 20 modules, transistor and circulator included, **487€/module**

For 150 modules, transistor and circulator included, **382€/module**

# Many thanks!

- To my colleagues of both the RF group and the design office, for their support.
- To Francis PEREZ (ALBA) who first dared to test the cavity combiner concept to combine 2 IOTs.